

# CENG 251: ELECTRIC CIRCUIT ANALYSIS AND DESIGN

---

Gidphil Mensah

# Content

- Basic Concepts
- Basic Laws
- Methods of Analysis
- Circuit Theorems
- Capacitors and Inductors
  - First – Order Circuits
  - Second – Order Circuits
- Laplace Transforms
- Operational Amplifiers
- Passive and Active Filters

# Assessment

- Continuous assessment – 40 marks
  - Weekly quizzes and assignments - 20 marks
  - Mid-semester examination – 20 marks
- End of semester examination – 60mks
  - Multiple choice questions – 20 marks
  - Written examination – 40 marks

# Further study

- Fundamentals of Electric Circuits (5<sup>th</sup> Edition): Charles K. Alexander, Matthew N. O. Sadiku, 2013.

[Click here for lecture materials](#)

# Basic Concepts


---

# Basic Electrical Quantities

Quantity	Unit	Basic equation
<b>Electric current (I):</b> the time rate of change of charge.	amperes (A)	$i \triangleq \frac{dq}{dt}$ $q$ – charge (C) t – time (s)
<b>Voltage / potential difference (V):</b> the energy required to move a unit charge through an element.	volts (V)	$v_{ab} \triangleq \frac{dw}{dq}$ $w$ – energy (J) $q$ – charge (C)
<b>Power (P):</b> the time rate of expending or absorbing energy.	watts (W)	$P = V \cdot I$
<b>Energy (E)</b> the capacity to do work.	joules (J)	$w = \int_{t_0}^t p \, dt = \int_{t_0}^t vi \, dt$
<b>Resistance (R):</b> the physical property of an element or device that impedes the flow of current.	ohms ( $\Omega$ )	$R = \frac{V}{I}$

# Circuit Elements

- An element is the basic building block of a circuit
- **Circuit analysis** is the process of determining voltages across (or the currents through) the elements of the circuit.
- There are two types of elements, namely (1) passive element and (2) active element
- An active element generates energy, while a passive element does not generate energy.
- The most important active elements are voltage or current sources that generally deliver power to the circuit connected to them.
- There are two kinds of sources: independent and dependent sources.
- An **ideal independent source** provides a specified voltage or current that is completely independent of other circuit elements.
- An ideal dependent (or controlled) source is an active element in which the source quantity is controlled by another voltage or current.
- Dependent sources are usually designated by diamond-shaped symbols as shown in Fig. 1.
- There are four possible types of dependent sources, namely:
  1. A voltage-controlled voltage source (VCVS)
  2. A current-controlled voltage source (CCVS)
  3. A voltage-controlled current source (VCCS)
  4. A current-controlled current source (CCCS)

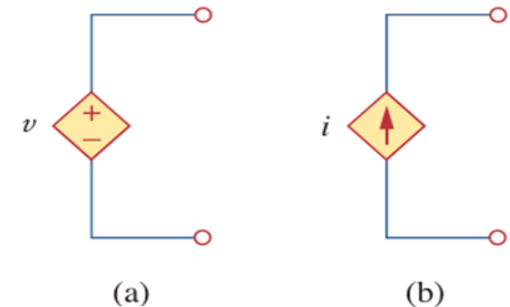

**Figure 1**

Symbols for: (a) dependent voltage source, (b) dependent current source.

# Circuit Elements



Independent voltage source



Independent current source



Dependent voltage source



Dependent current source



Diode




Capacitor



Inductor



Resistor

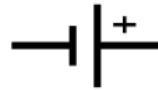

DC voltage source



AC voltage source



Variable resistor



# Basic Laws

---

# Ohm's Law


- **Ohm's law** states that the voltage  $v$  across a resistor is directly proportional to the current  $i$  flowing through the resistor.

$$v \propto i$$
$$v = iR$$

- The resistance of any material with a uniform cross-sectional area  $A$ , depends on  $A$  and its length  $l$ , as shown in Fig. 2.

$$R = \rho \frac{\ell}{A}$$

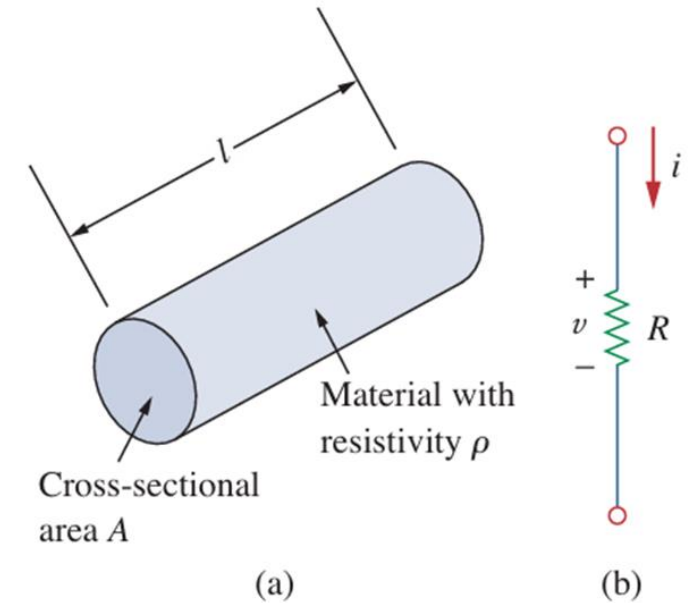- Where  $\rho$  is the resistivity of the material in ohm-meters.
- Conductance  $G$  is a measure of how well an element will conduct electricity, measured in mho (ohm spelled backwards).
- It's the reciprocal of  $R$ .  $G = \frac{1}{R}$ , unit  $\mathcal{U}$ , SI unit is siemens (S).


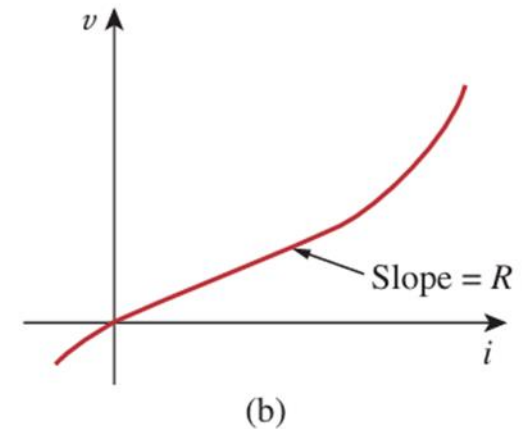


**Figure 2**

(a) Resistor, (b) Circuit symbol for resistance.
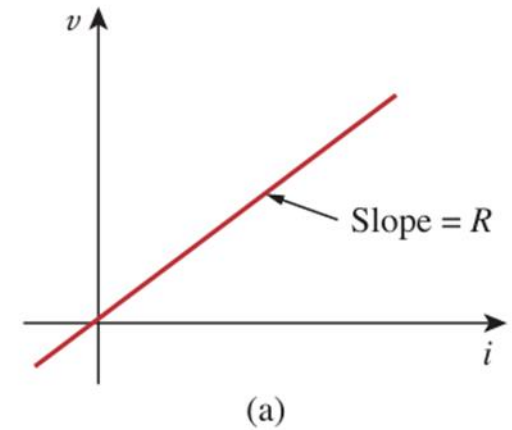
# Ohm's Law


- It should be noted that not all resistors obey Ohm's law.
- A resistor that obeys Ohm's law is known as a linear resistor and has  $i$ - $v$  characteristics as shown in Figure (a).
- A nonlinear resistor does not obey Ohm's law. Its resistance varies with current and its  $i$ - $v$  characteristic is typically shown in Figure (b).



The  $i$ - $v$  characteristic of: (a) a linear resistor, (b) a nonlinear resistor.


# Branches, Nodes, and Loops

- A **branch** represents a single element.
- A **node** is the point of connection between two or more branches.
- A **loop** is any closed path in a circuit.
- Fig. 3 can be redrawn as Fig. 4 by combining the nodes connected by conducting wires.
- Two or more elements are in **series** if they exclusively share a single node and consequently carry the same current.
- Two or more elements are in **parallel** if they are connected to the same two nodes and consequently have the same voltage across them.

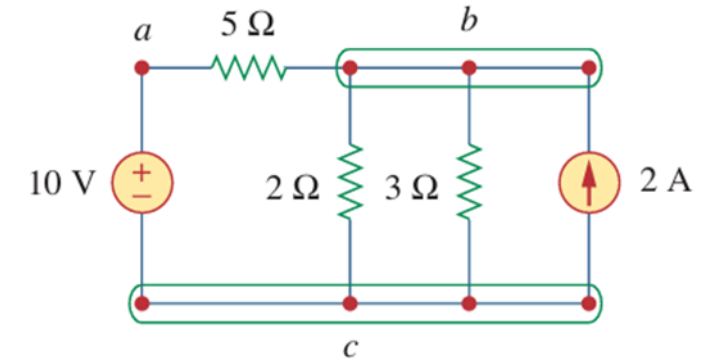

**Figure 3**

Nodes, branches, and loops.

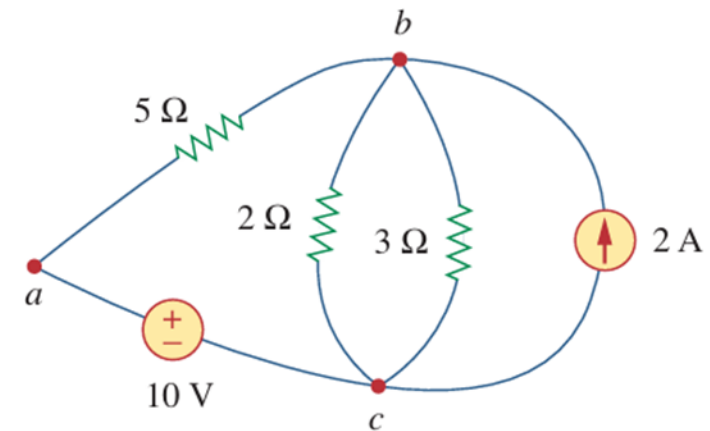



**Figure 4**

The three-node circuit of Fig. 2.10 is redrawn.

# Branches, Nodes, and Loops
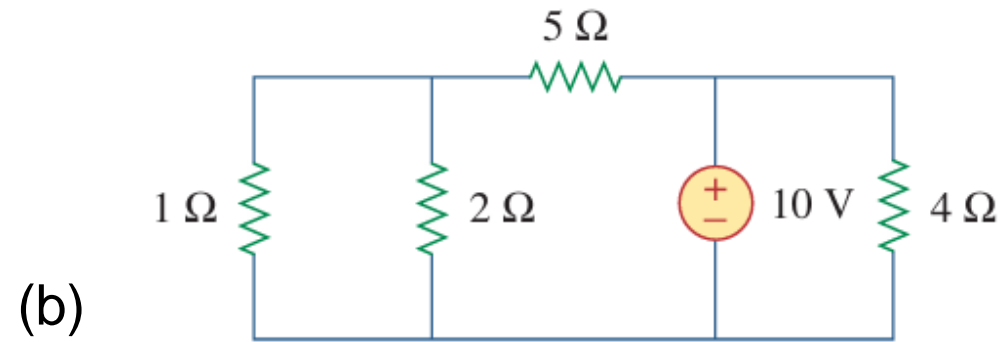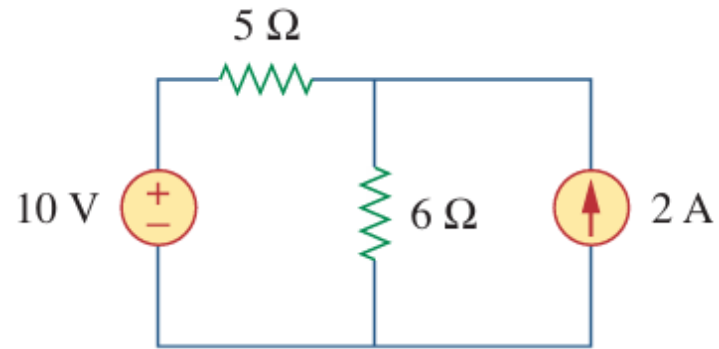
## Problem

- Determine the number of branches and nodes in the circuits shown below. Identify which elements are in series and which are in parallel.



# Kirchhoff's Laws


- Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.
- The sum of the currents entering a node is equal to the sum of the currents leaving the node.

$$i_1 + i_3 + i_4 = i_2 + i_5$$


- In Fig. 2.17, the total current entering the closed surface is equal to the total current leaving the surface.

- KCL can be applied to current sources in parallel such that


$$I_T = I_1 - I_2 + I_3$$

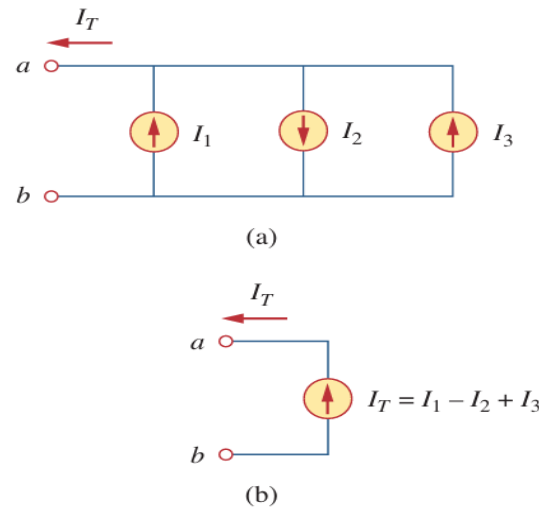

**Figure 2.18**  
Current sources in parallel: (a) original circuit, (b) equivalent circuit.

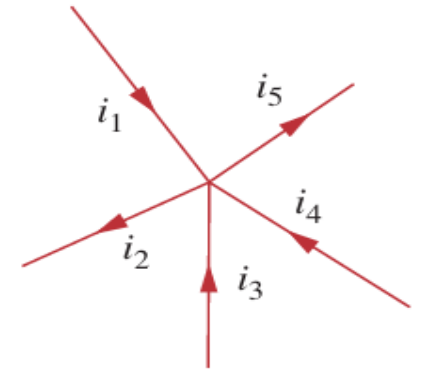

**Figure 2.16**  
Currents at a node illustrating KCL.

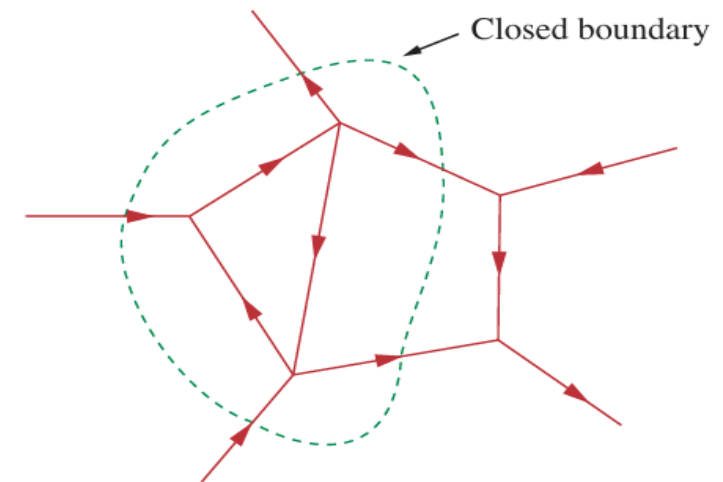

**Figure 2.17**  
Applying KCL to a closed boundary.

# Kirchhoff's Laws

- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.
- Consider the circuit in Fig. 2.19. The sign on each voltage is the polarity of the terminal encountered first as we travel around the loop.


$$\begin{aligned} -v_1 + v_2 + v_3 - v_4 + v_5 &= 0 \\ v_1 + v_4 &= v_2 + v_3 + v_5 \end{aligned}$$

- In other words,

*Sum of voltage drops = Sum of voltage rises*


- In Fig. 2.20, KVL can be applied to voltage sources in series such

$$V_{ab} = V_1 + V_2 - V_3$$

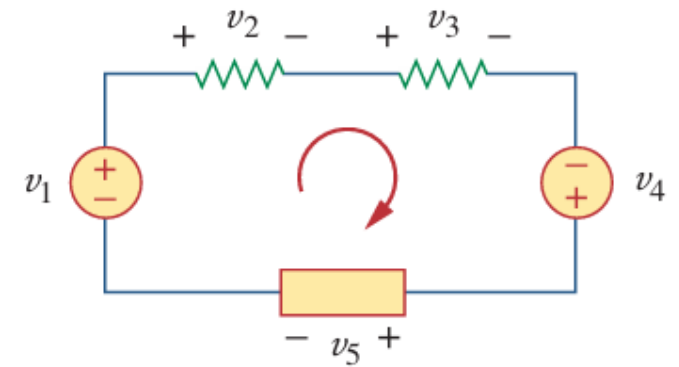

**Figure 2.19**

A single-loop circuit illustrating KVL.

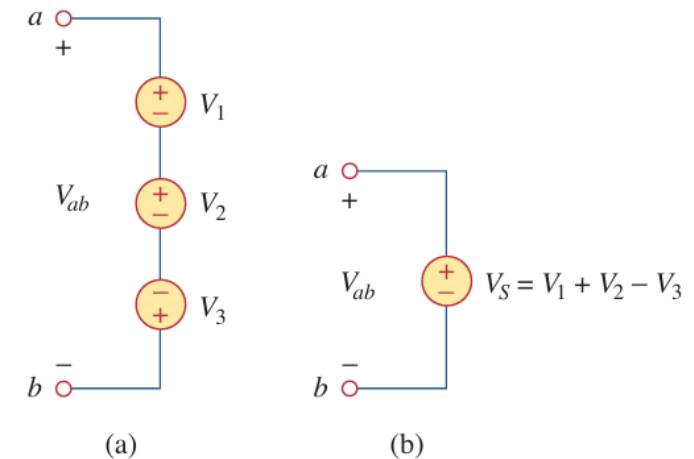


**Figure 2.20**

Voltage sources in series: (a) original circuit, (b) equivalent circuit.


# Kirchhoff's Laws
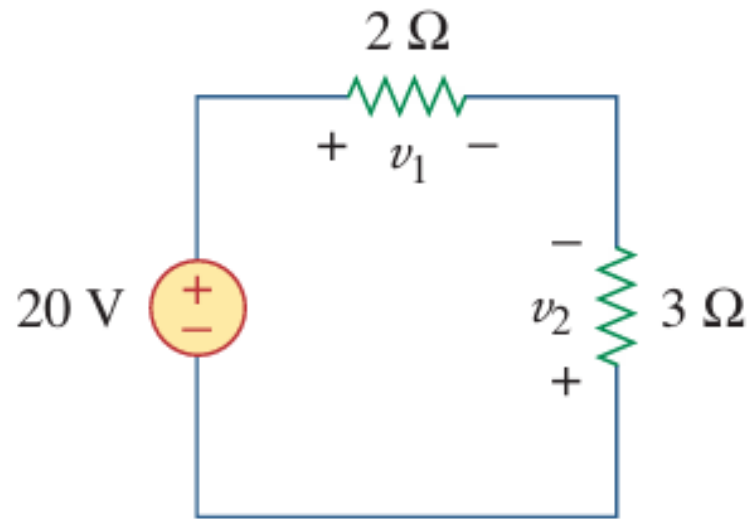
## Problems

For the circuits below, find voltage  $v_1$  and  $v_2$ .




(a)

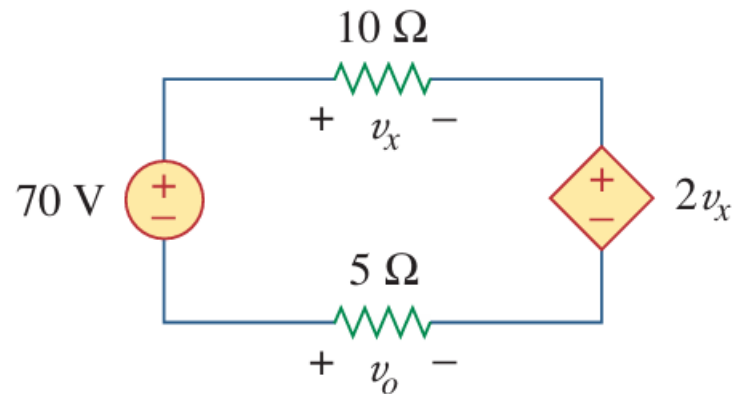

For the circuits below, find voltage  $v_x$  and  $v_o$ .

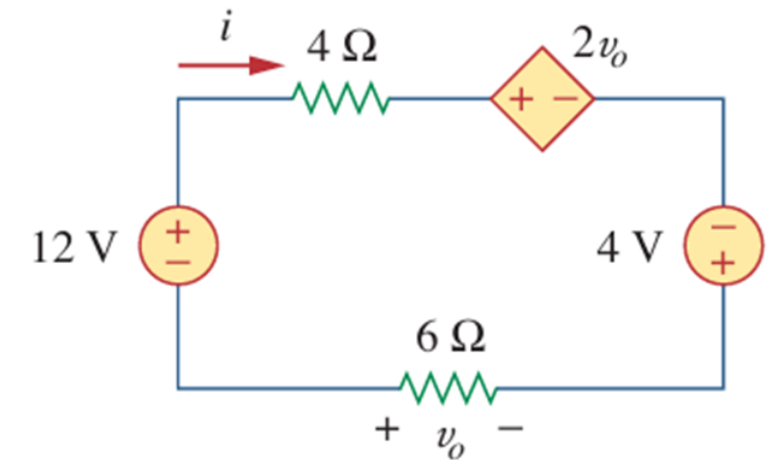Determine  $v_o$  and  $i$  in the circuit below



(b)



# Series Resistors and Voltage Division

- For two resistors in series as shown in Fig. 2.29

$$R_{eq} = R_1 + R_2$$


- The equivalent resistance of any number of resistors connected in series is the sum of the individual resistances.
- Per the voltage divider rule, the source voltage  $v$  is divided among the resistors in direct proportion to their resistances.

$$v_1 = \frac{R_1}{R_1 + R_2} v$$

$$v_2 = \frac{R_2}{R_1 + R_2} v$$

- In general, if a voltage divider has  $N$  resistors ( $R_1, R_2, R_3, \dots, R_N$ ) in series with the source voltage  $v$ , the  $n$ th resistor ( $R_n$ ) will have a voltage drop of

$$v_n = \frac{R_n}{R_1 + R_2 + R_3 + \dots + R_N} v$$

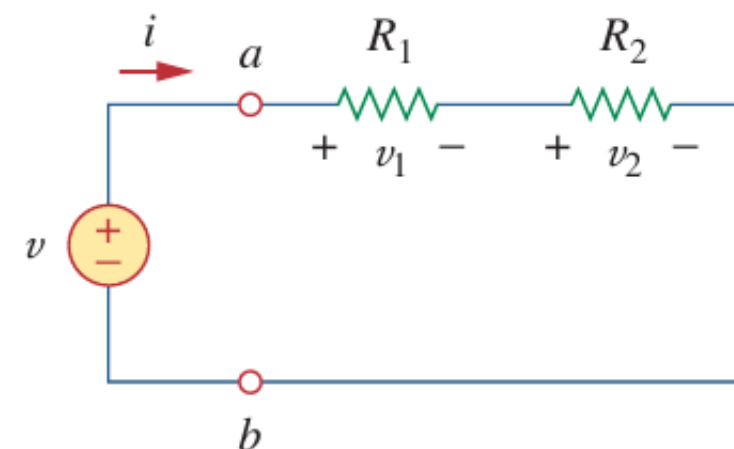

**Figure 2.29**

A single-loop circuit with two resistors in series.

# Parallel Resistors and Current Division

- For two resistors in parallel as shown in Fig. 2.31.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$


- In the general case of a circuit with N resistors in parallel. The equivalent resistance is

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$

- Per the current divider rule,

$$i_1 = \frac{R_2}{R_1 + R_2} i$$
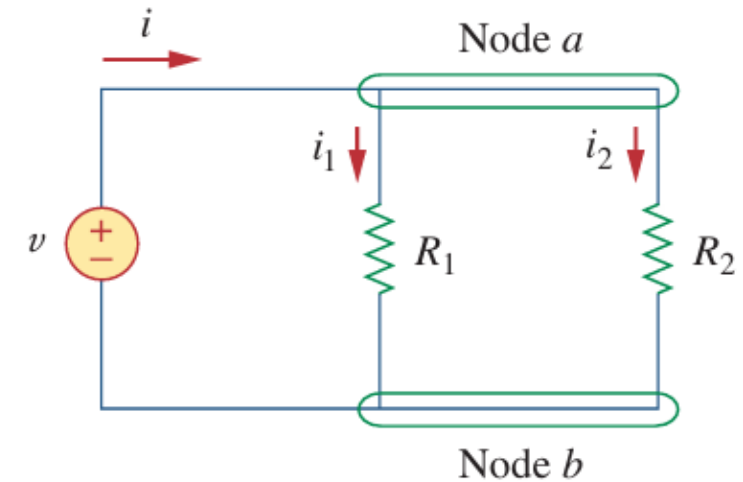
$$i_2 = \frac{R_1}{R_1 + R_2} i$$


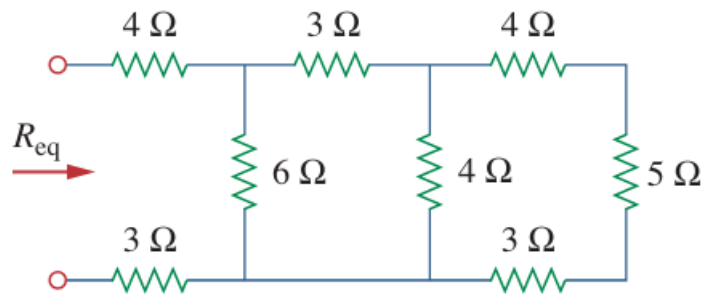
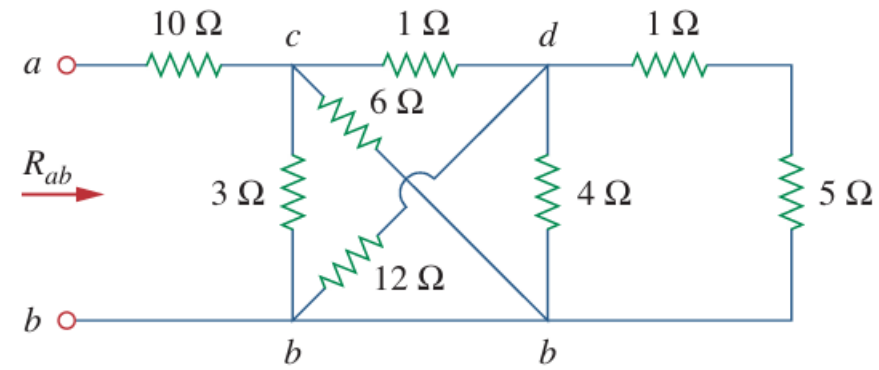


**Figure 2.31**

Two resistors in parallel.
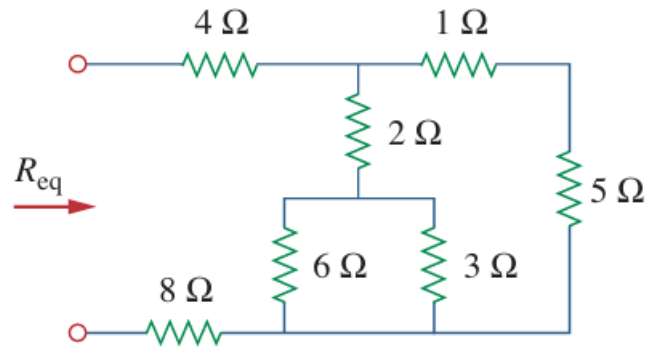
# Problems

- Find the equivalent resistances of the circuits shown below



# Methods of Analysis

---

# Nodal Analysis


## • Nodal Analysis with only current sources

### Steps to Determine Node Voltages:

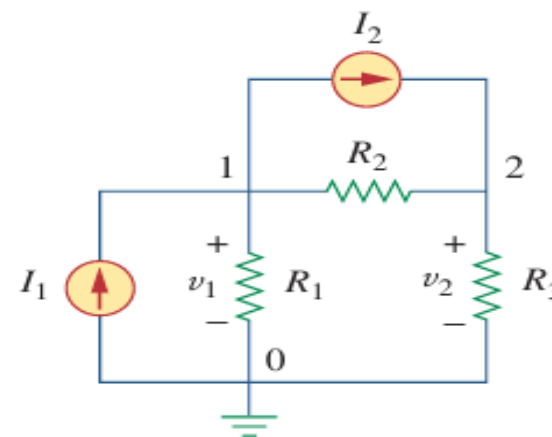
1. Select a node as the reference node. Assign voltages  $v_1, v_2, \dots, v_{n-1}$  to the remaining  $n - 1$  nodes. The voltages are referenced with respect to the reference node.
2. Apply KCL to each of the  $n - 1$  nonreference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
3. Solve the resulting simultaneous equations to obtain the unknown node voltages.

- Current flows from a higher potential to a lower potential in a resistor.

$$i = \frac{v_{\text{higher}} - v_{\text{lower}}}{R}$$



(a)

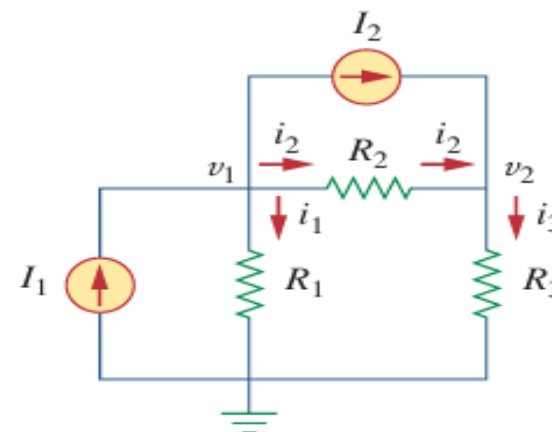

(b)

At node 1,

$$I_1 = I_2 + i_1 + I_2$$

$$I_1 = I_2 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2}$$

At node 2,

$$I_2 = i_3 + i_3$$

$$I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3}$$


**Figure 3.2**

Typical circuit for nodal analysis.


# Nodal Analysis
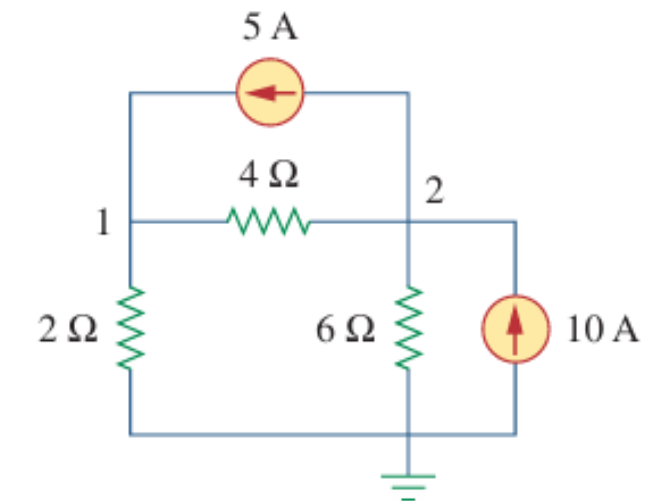
## • Problems

Calculate the node voltages in the circuits (a) and (b)




(a)

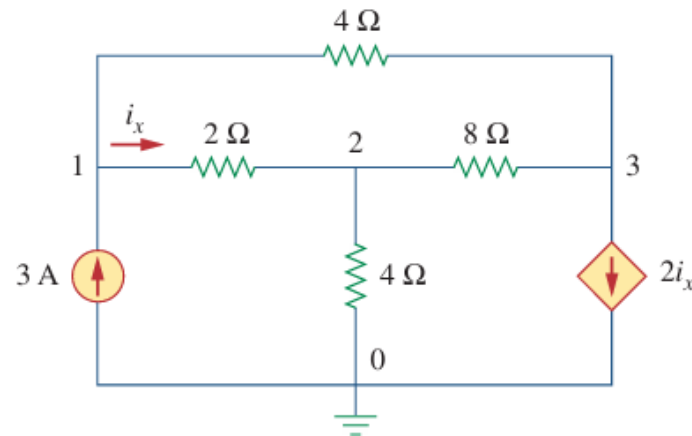

(b)

- **Assignment 1** – (Deadline: Thursday Jan 16, 2025, 23:59)

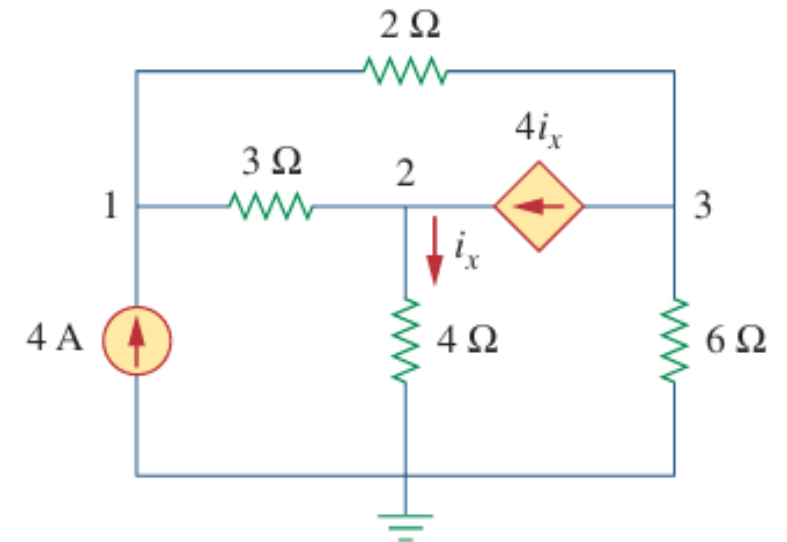
Determine the voltage at the three non-reference nodes



# Nodal Analysis with Voltage Source

- **Nodal Analysis with voltage sources**
- CASE1: If a voltage source is connected between the reference node and a nonreference node, simply set the voltage at the non reference node equal to the voltage of the voltage source.
- In Fig. 3.7, for example,  $v_1 = 10\text{ V}$ .
- CASE 2: If the voltage source (dependent or independent) is connected between two non-reference nodes, the two non-reference nodes form a **supernode**, apply both KCL and KVL to determine the node voltages.

A supernode is formed by enclosing a (dependent or independent) voltage source connected between two nonreference nodes and any elements connected in parallel with it.

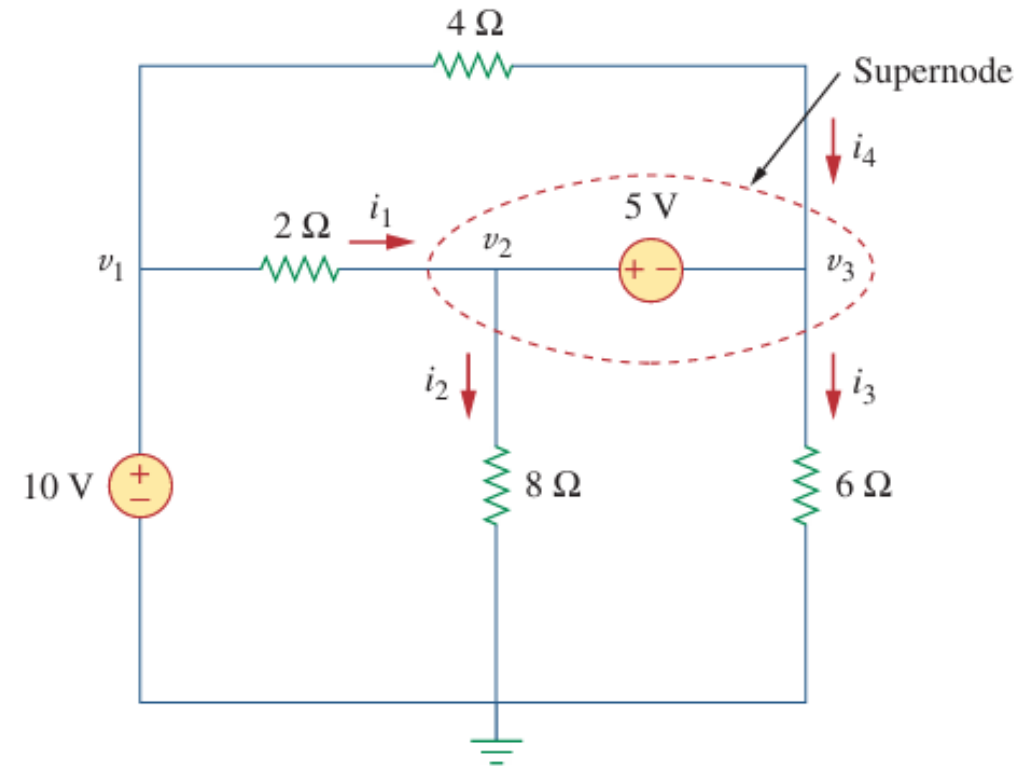

**Figure 3.7**  
A circuit with a supernode.

# Nodal Analysis with Voltage Source


- At the supernode,

$$i_1 + i_4 = i_2 + i_3$$

$$\frac{v_1 - v_2}{2} + \frac{v_1 - v_3}{4} = \frac{v_2 - 0}{8} + \frac{v_3 - 0}{6}$$

- Applying KVL to the supernode,

$$-v_2 + 5 + v_3 = 0 \quad \Rightarrow \quad v_2 - v_3 = 5$$

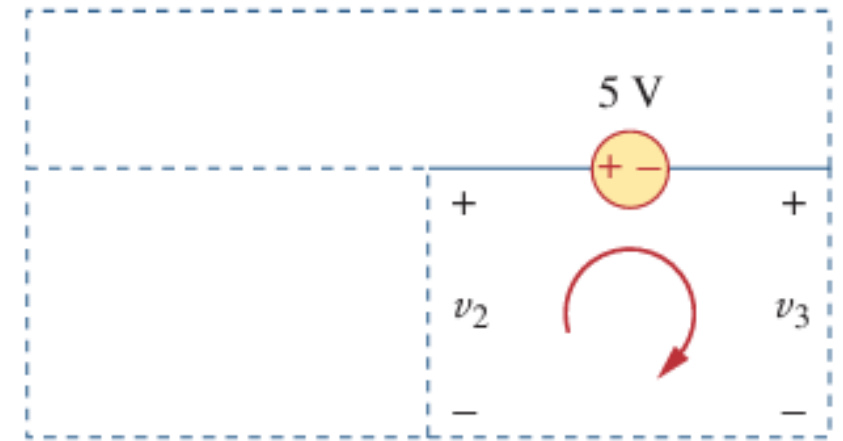

**Figure 3.8**



Applying KVL to a supernode.



# Nodal Analysis with Voltage Source

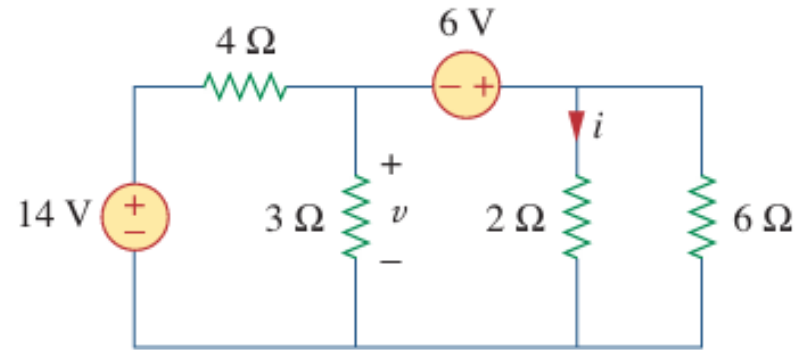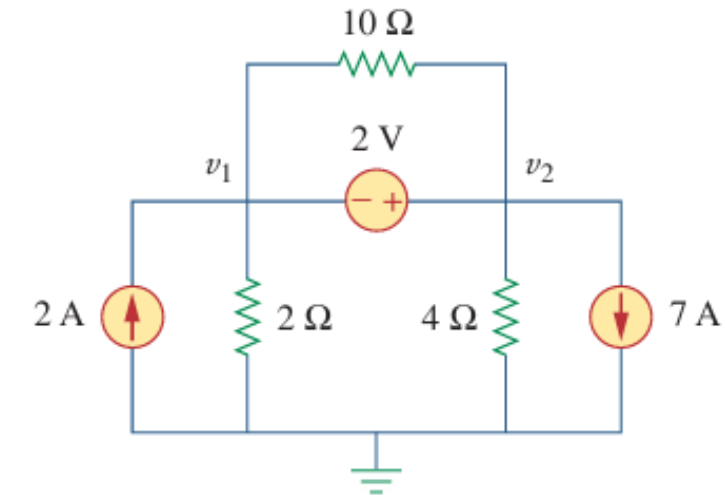
## Problems

Find the node voltages in the circuit below



Find  $v$  and  $i$ .
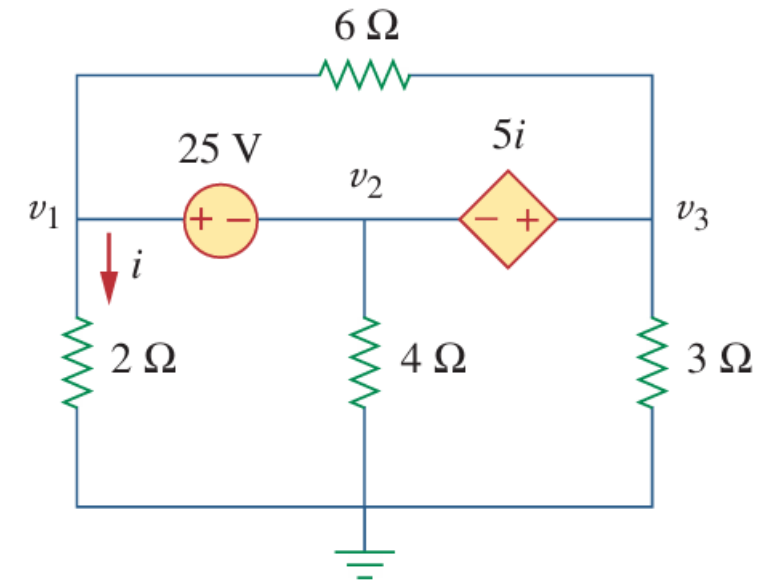
## Assignment 2 – (Deadline: Sunday, Jan 19, 2025, 20:00)




Using nodal analysis, find  $v_1$ ,  $v_2$ , and  $v_3$  in the circuit above

# Mesh Analysis

- A mesh is a loop which does not contain any other loops within it.

## Steps to Determine Mesh Currents:

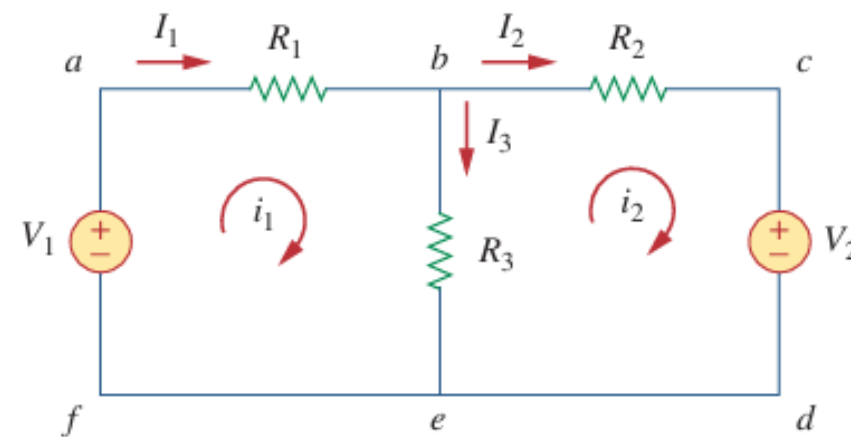1. Assign mesh currents  $i_1, i_2, \dots, i_n$  to the  $n$  meshes.
2. Apply KVL to each of the  $n$  meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the resulting  $n$  simultaneous equations to get the mesh currents.



Applying KVL to mesh 1

$$-V_1 + R_1 i_1 + R_3(i_1 - i_2) = 0$$

$$(R_1 + R_3)i_1 - R_3 i_2 = V_1$$


Applying KVL to mesh 2

$$R_2 i_2 + V_2 + R_3(i_2 - i_1) = 0$$


$$-R_3 i_1 + (R_2 + R_3)i_2 = -V_2$$

# Mesh Analysis

## Problems

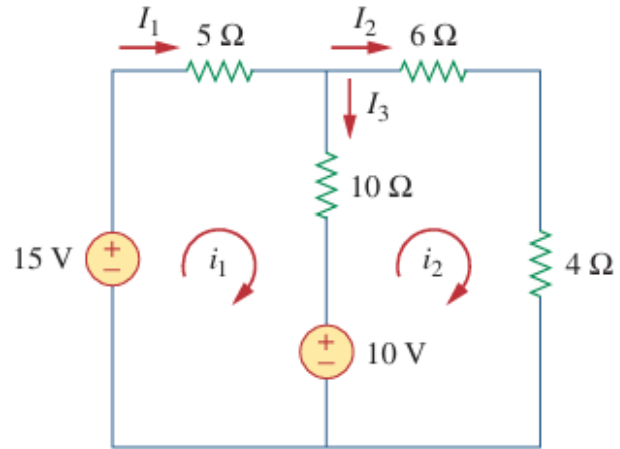

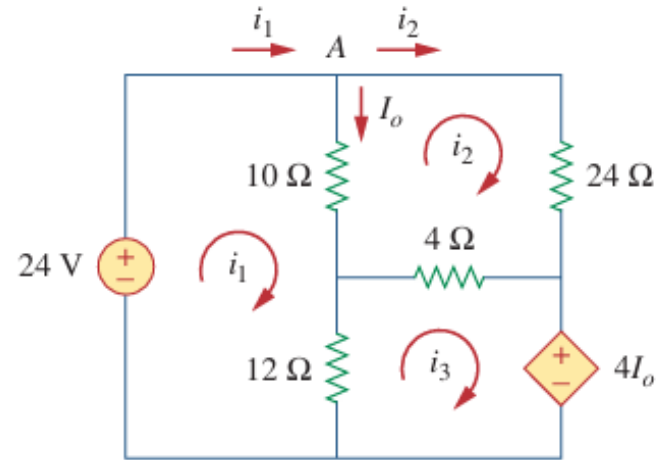Find the branch currents using mesh analysis.




Use mesh analysis to find the mesh currents in the circuit

# Mesh Analysis with Current Sources

- CASE 1: When a current source exists only in one mesh: Consider the circuit in Fig. 3.22 for example, set  $i_2 = -5\text{ A}$  and write a mesh equation for the other mesh in the usual way.

$$-10 + 4i_1 + 6(i_1 - i_2) = 0 \quad \Rightarrow \quad i_1 = -2\text{ A}$$

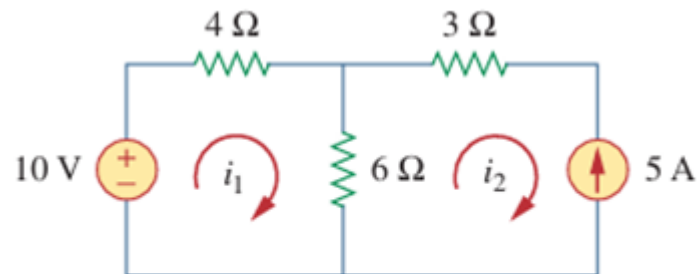


**Figure 3.22**

A circuit with a current source.

- CASE 2: When a current source exists between two meshes: Consider the circuit in Fig. 3.23(a), for example. Create a supermesh by excluding the current source and any elements connected in series with it, as shown in Fig. 3.23(b).

**A supermesh results when two meshes share a current source (dependent or independent).**

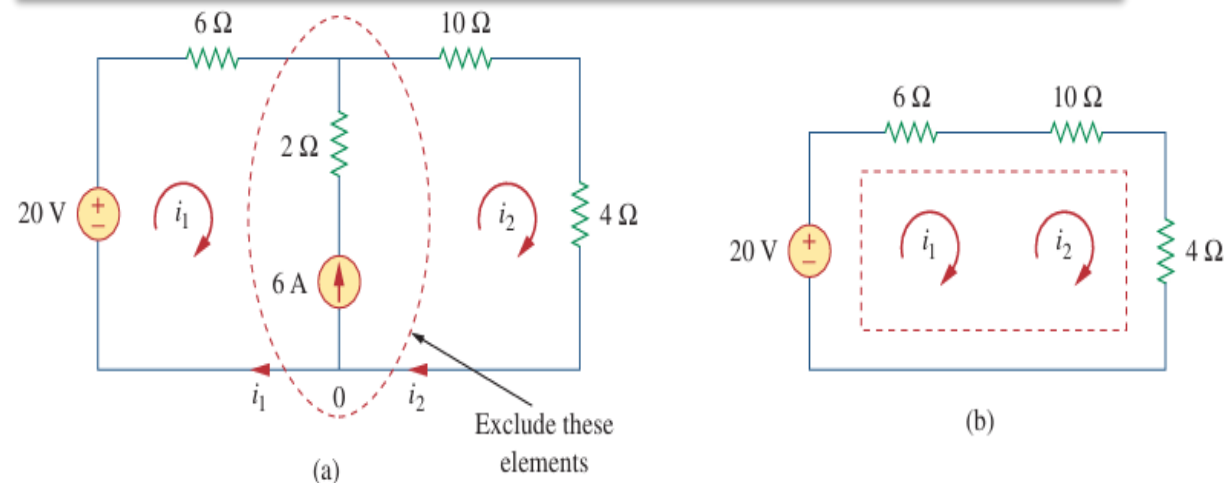

**Figure 3.23**

(a) Two meshes having a current source in common, (b) a supermesh, created by excluding the current source.

$$-20 + 6i_1 + 10i_2 + 4i_2 = 0$$

$$6i_1 + 14i_2 = 20 \quad (1)$$

apply KCL to the node where the two meshes meet.

$$i_2 = i_1 + 6 \quad \text{OR} \quad i_2 - i_1 = 6 \quad (2)$$


Solving equation (1) and (2) simultaneously,

$$i_1 = -3.2\text{ A} \quad i_2 = 2.8\text{ A}$$


# Mesh Analysis with Current Sources
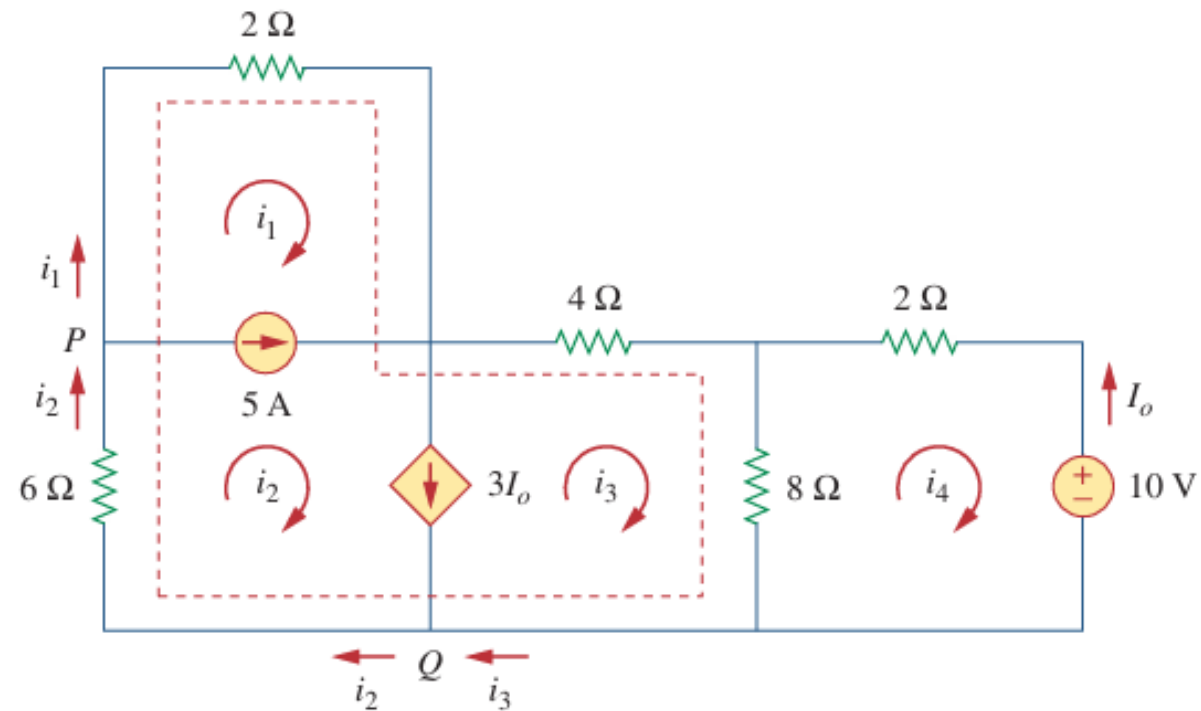
## Problems

Use mesh analysis to determine  $i_1$ ,  $i_2$ ,  $i_3$  and  $i_4$  in the circuit below.


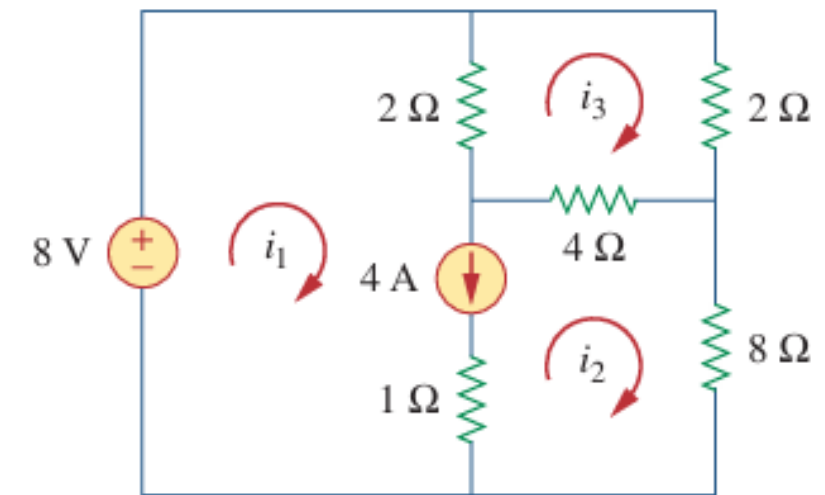
## Assignment 3 – (Deadline: Tuesday, Jan 28, 2025, 23:59)



Use mesh analysis to determine  $i_1$ ,  $i_2$  and  $i_3$  in the circuit above.

# Nodal Analysis vs. Mesh Analysis

## Difference between modal analysis and mesh analysis

Nodal analysis	Mesh analysis
Used to find node voltages	Used to find branch and mesh currents
Can solve non-planar circuits	Cannot solve non-planar circuit
Primarily depends on KCL	Primarily depends on KVL
A supernode is when a voltage source is found in between two non-reference nodes	A supermesh is when a current source is shared by two meshes
Supernode is secondarily solved using KVL	Supermesh is secondarily solved using KCL